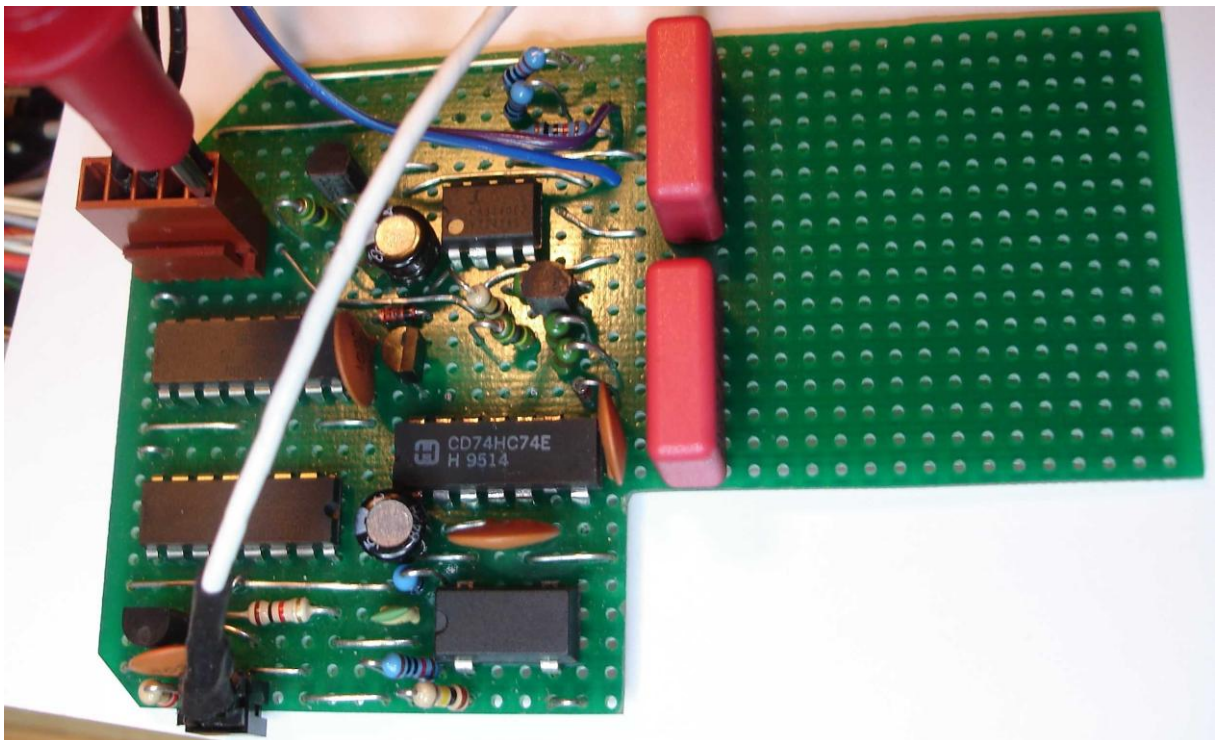


A Huf-Puf VFO stabilizer for the YAESU FT-707




VFO Stabilizer for the Yaesu FT-707


The white circles represent track cuts. Black lines are blank connection wires. Black dots on these lines are through-hole connections. Gray lines are also blank connection wires, but on the other side of the pcb. The yellow wire is isolation. Note the two green dots at the bottom for the reset switch. I don't claim the design to be optimal. Of course you can design your own pcb.

Note also that only the part containing components is shown, not the empty area intended for mounting purposes.

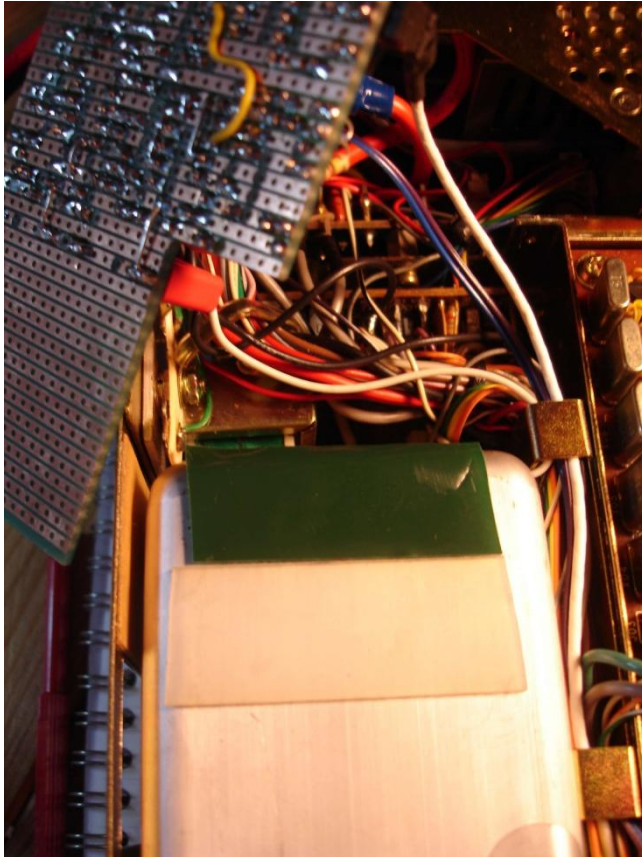
The PCB is mounted upside down on the location where the speaker used to sit. It is fixed with double sided tape on top of the VFO housing.



VFO Stabilizer for the Yaesu FT-707

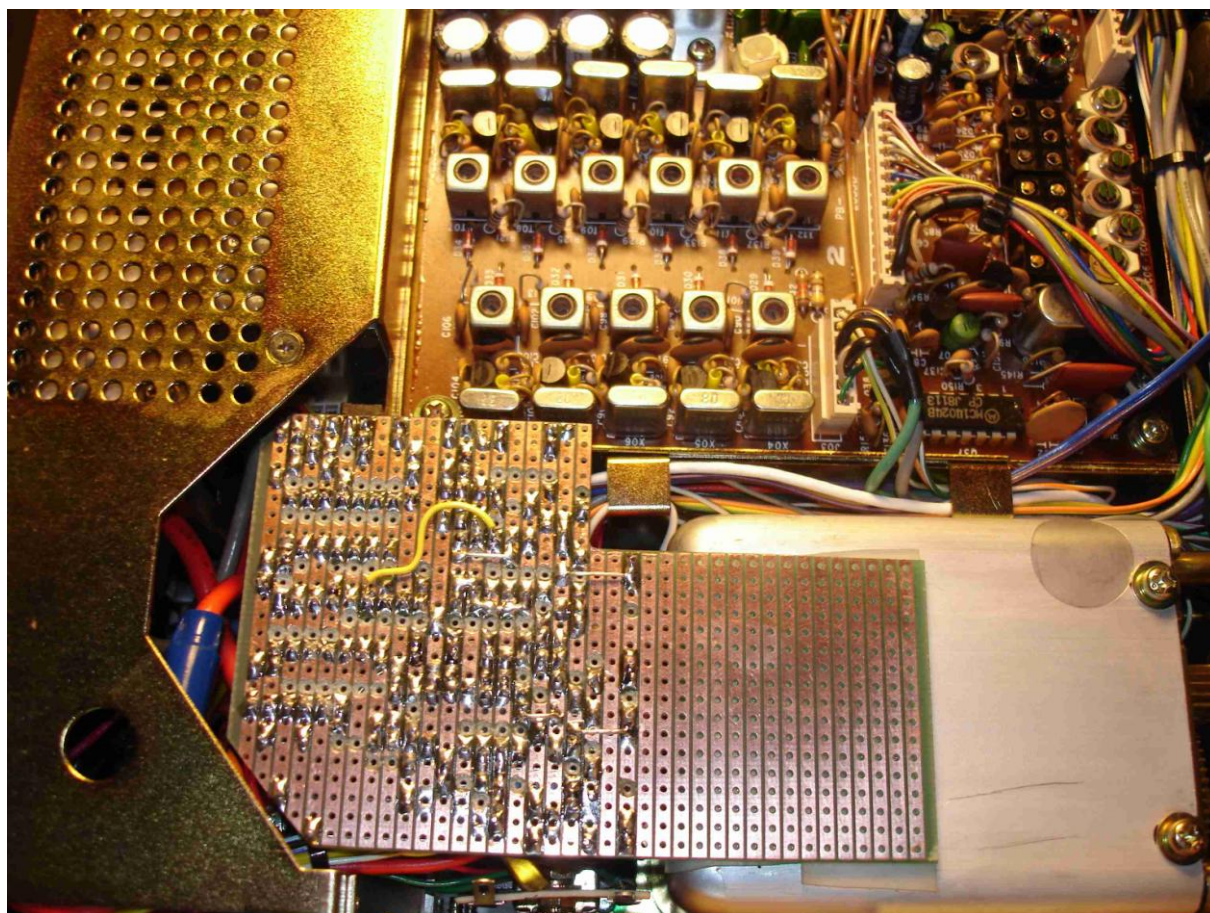

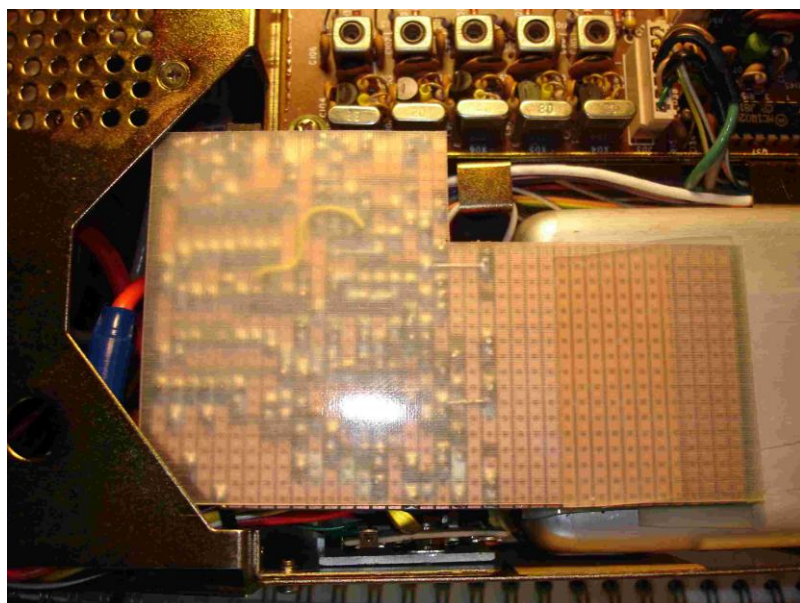The stabilizer PCB does not touch the bottom cover at all, but to be safe, I mounted a protective transparent cover, also with a strip of double sided tape.



With the double sided tape, the stabilizer is VERY firmly fixed, in fact you will have to take care not to break the pcb if you want to remove it again!


VFO Stabilizer for the Yaesu FT-707

The “reset button” :

I already used the “FIX” button for an “attenuator mod”. This really is a MUST on the low bands so I advise to keep it available for this purpose. Other push-buttons cannot be sacrificed.

I really hate drilling holes in nice transceiver housings. So the issue was solved by using the “mode” switch. By turning it to the “AM” position and back, the VFO stabilizer is reset via an added 12V relay.

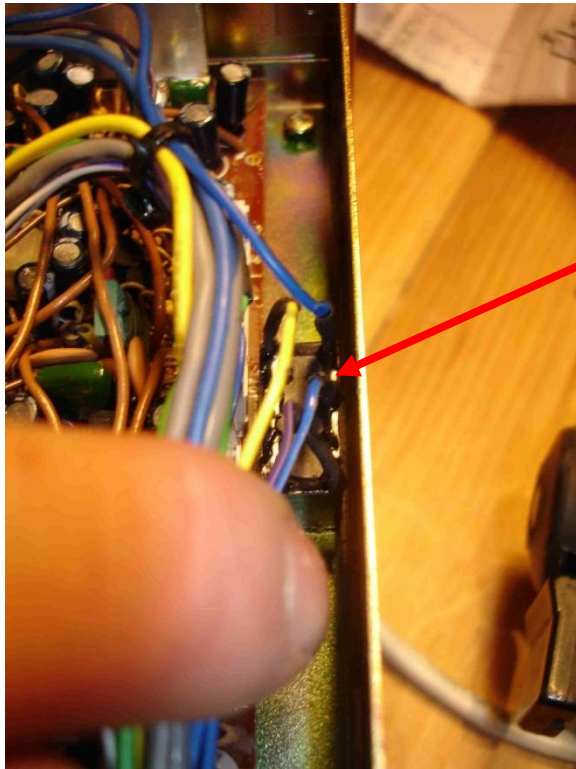This implies it is not working in AM (as it is continuously reset) but then again, who needs a VFO stabilizer in AM mode?




Reset relais
Mounted upside down aside the
AF board

VFO Stabilizer for the Yaesu FT-707

Signals needed for the stabilizer and where to get them:

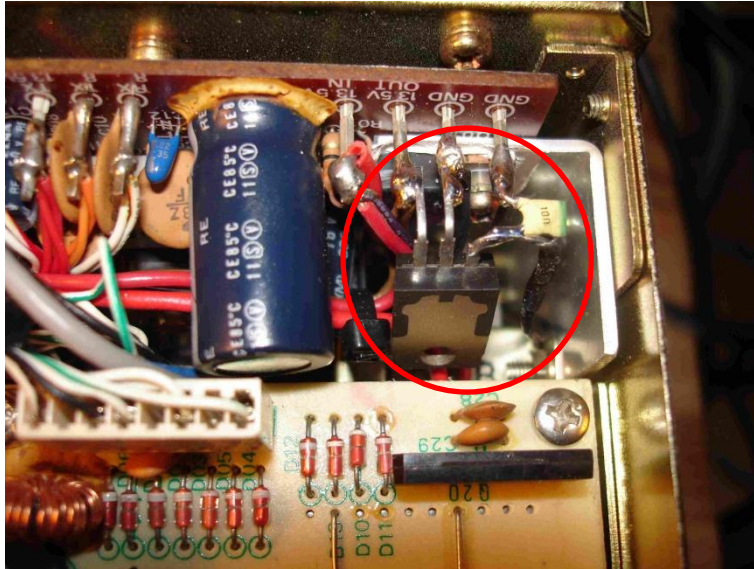- **8V:** Don't use the stabilised 8V of the FT707. It is not stable enough. The stabilizer will jump now and then. Use an extra 7808 stabilizer IC. This can be mounted very neatly on the AVR PCB behind the counter PCB.



- **Ground:** just behind the VFO on the AVR pcb.
- **VFO signal:** NOT on the VFO connector as this is quite fragile. I got it from the underside of the connector on the RF PCB where the VFO signal is brought in and routed it down to the stabilizer.
- **VARICAP DIODE:** I initially used the varicap circuit already there for the clarifier (1S2236). I simply cut the gray wire going from the clarifier pot to the VFO connector and connected the stabilizer to it. This has several advantages:
 - o We know this varicap circuit works, so we can eliminate that error-possibility if we should have problems with the stabilizer.
 - o We don't have to go into the VFO in order to test the stabilizer.
 - o If the circuit works ok with the clarifier Varicap and if you feel you can do without a clarifier, that's the end of the job. Otherwise you can install a new separate varicap for the stabilizer and use the original varicap for the clarifier again so you will have no clarifier alignment issues. This involves opening the VFO unit and some soldering inside. Not very difficult, but a job needing care and precision.

Adding a separate stabilizer varicap:

The varicap:

The proposed type in the schematic diagram by PA0FRI is a BB521. Because these were not obtainable at my location, I used a BB205 which has a range of 2pf – 17pf. Because of the lower capacitance values of a BB521, I still think this remains the preferred type.


VFO Stabilizer for the Yaesu FT-707

Mounting the components:

This involves opening the VFO unit. This can be done by :


- Removing the 4 screws fixing the front panel to the rest of the transceiver
- Removing the little strip where the loudspeaker connections are plugged on.
- Remove the connector to the VFO unit.
- Remove the counter pcb and it's base plate.

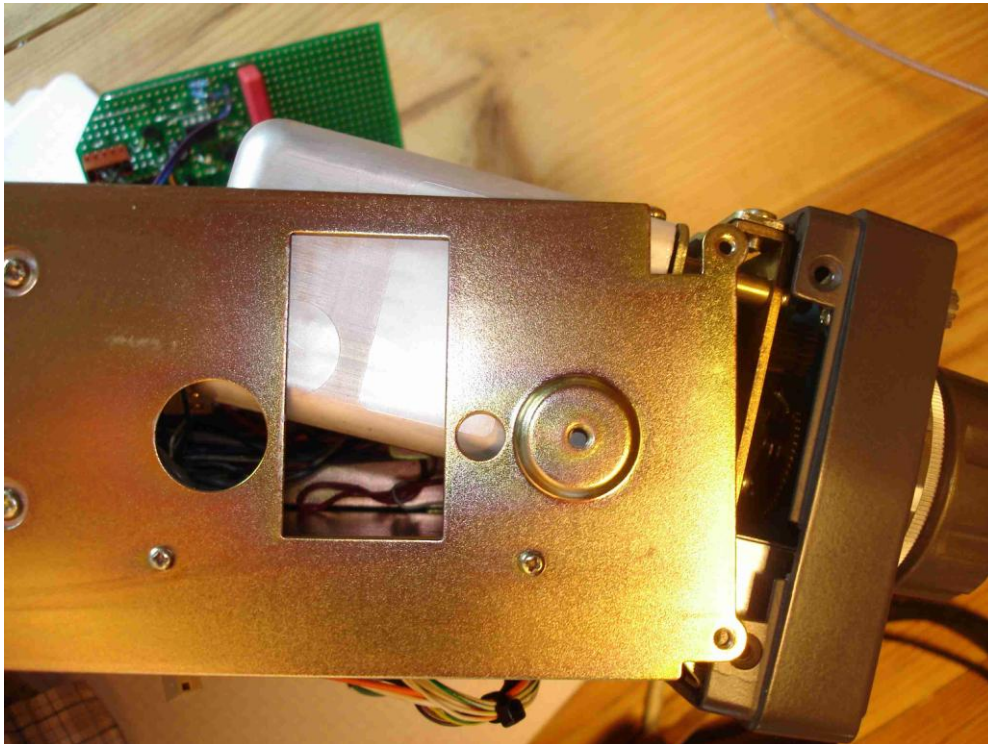The front panel can now be tilted far enough so the VFO housing can be slid-off after removing the 4 screws holding it.




To avoid further dismantling and to disturb the VFO the least possible, the BB205 varicap and the 6pf capacitor were mounted on the foil side of the pcb and connected to the 15pf adjustable trimmer.



VFO Stabilizer for the Yaesu FT-707

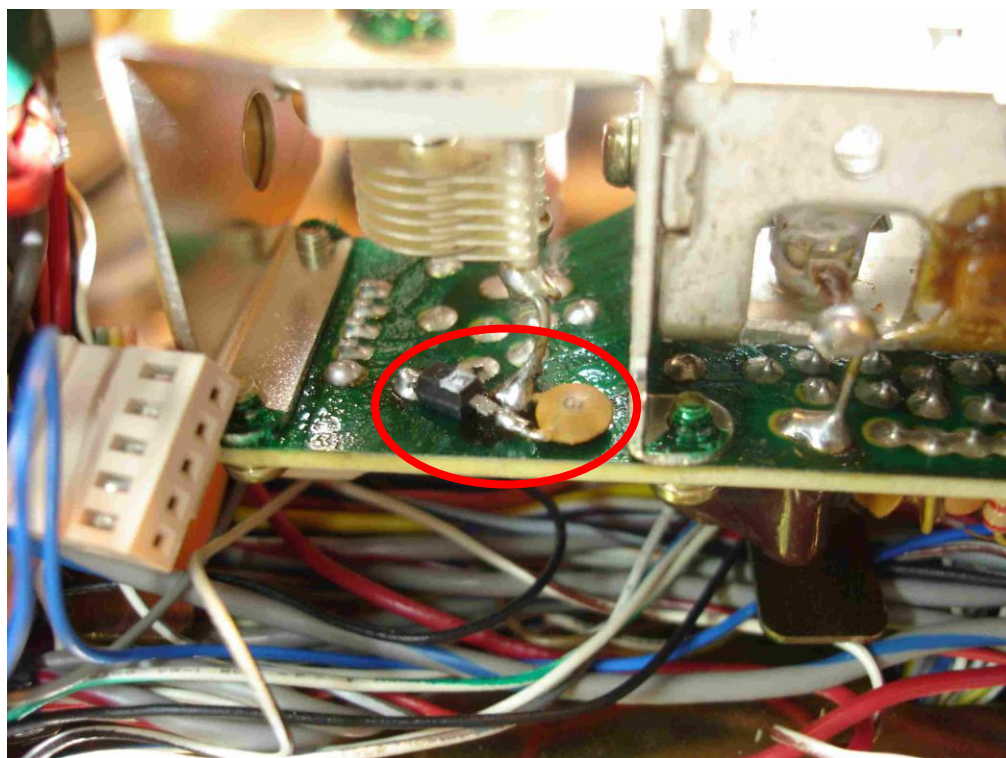

The rest of the circuit is mounted at the component side in order to avoid detuning as much as possible. To do so, two little slips are to be made in the side of the pcb to pass the component wires to the other side. With a Dremel tool, this is a quite straightforward job. All added components are glued to the pcb with epoxy glue to avoid any movement. Also the extra wire leaving the VFO assembly is glued to the pcb.

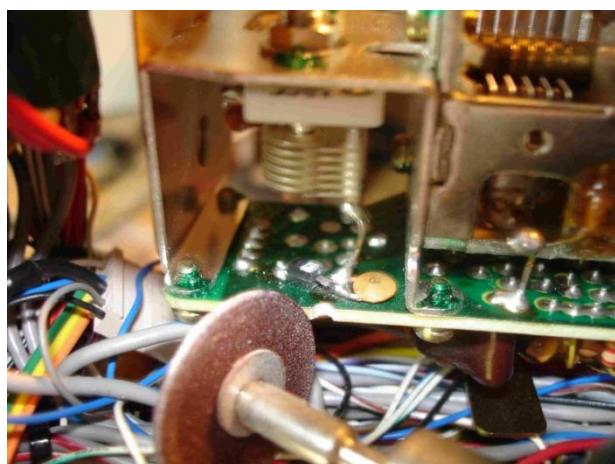

VFO Stabilizer for the Yaesu FT-707

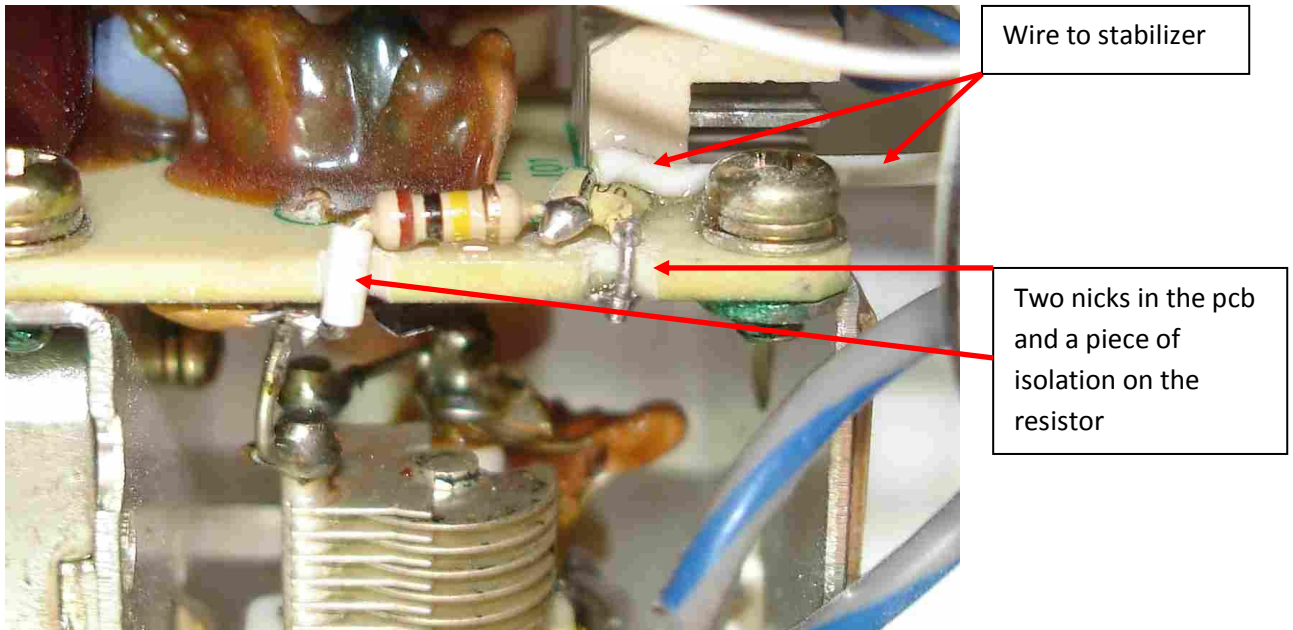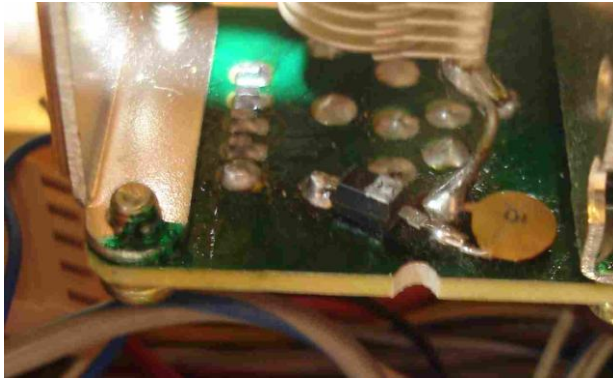

Re-alignment:

After finishing and reassembling the VFO again, the 15pf trimmer need readjustment because of the added varicap capacitance, otherwise the VFO range does not reach the lower part of the amateur bands. This can be done by partly removing the aluminum tape covering the adjustment hole at the side of the VFO.

Also, the main dial need readjustment, this can be done by loosening the screw of the appropriate cog-wheel.

A few critical point for the stabilizer:


- **The 7474 flip-flop IC.:**
 - This has to be a HC or HCT type. HC(T) types have a higher low-level input voltage. If you use other types, your oscillator signal might not go low enough to switch the flip-flop.

VFO Stabilizer for the Yaesu FT-707

- **The diodes at the base of the BC557/BC547 transistors:**
 - o There are some schematics going around on the internet where these are wrongly polarized.
- **The 1 microfarad capacitors:**
 - o These have to be low leakage. Preferred types are MKM or MKP.
 - o 1mmF as in the original design by PA0KSB or 2,2mmF types as in the PA0FRI design both work. The stabilizer is a little bit "faster" when using 1mmF types.
- **The reference oscillator:**
 - o As reference oscillator, I used a 48.000MHz chip which I desoldered from an old PC motherboard. The advantages over a regular Xtal oscillator with a coil are obvious:
 - o far less RF radiation into the receiver
 - o just a single component to mount
 - o a tiny footprint
 - o no adjustments
 - o no fuzz.

Schematics:


1- Huf Puf circuit diagram PA0FRI:

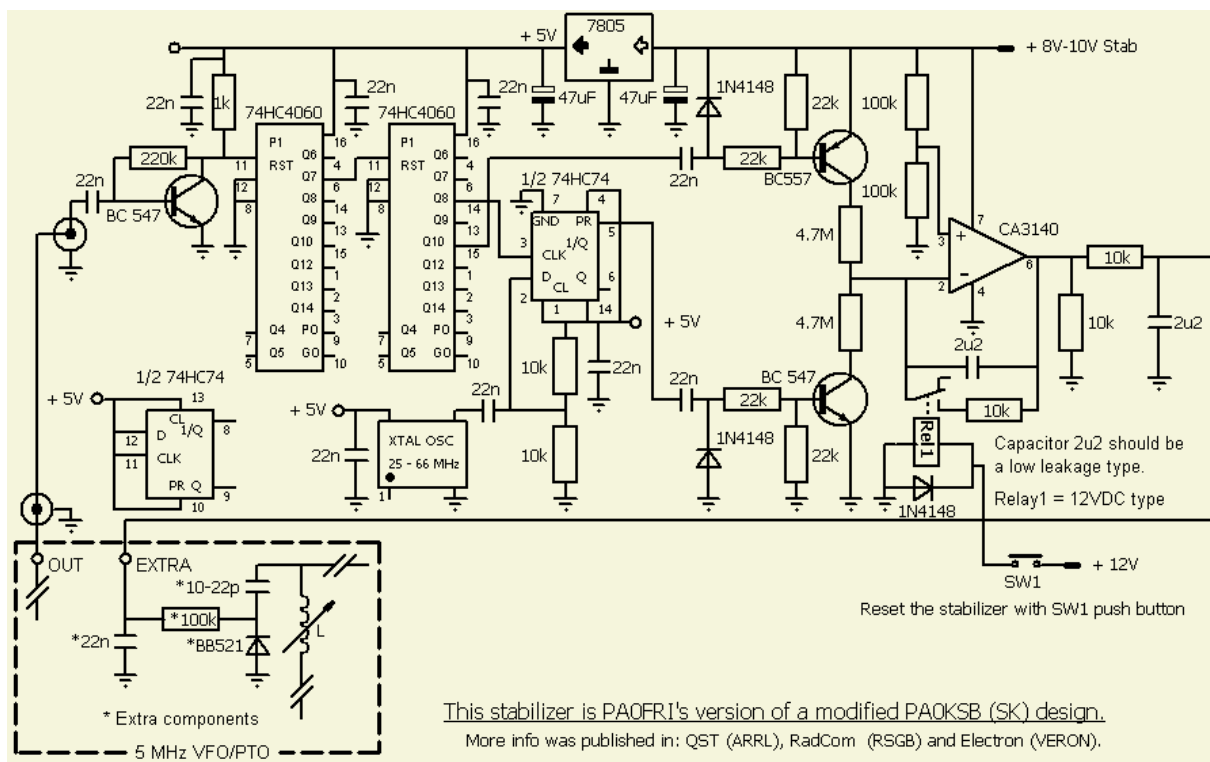


VFO Stabilizer for the Yaesu FT-707

Frequency locking steps:

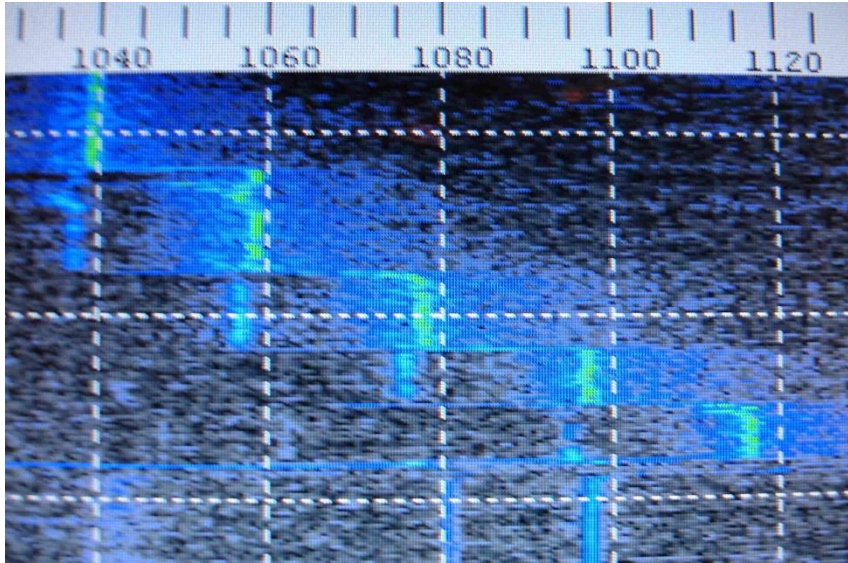With the FT707 VFO, the 48MHz reference and the used divider settings these are +/- 19Hz.




Frequency turn-on behavior:

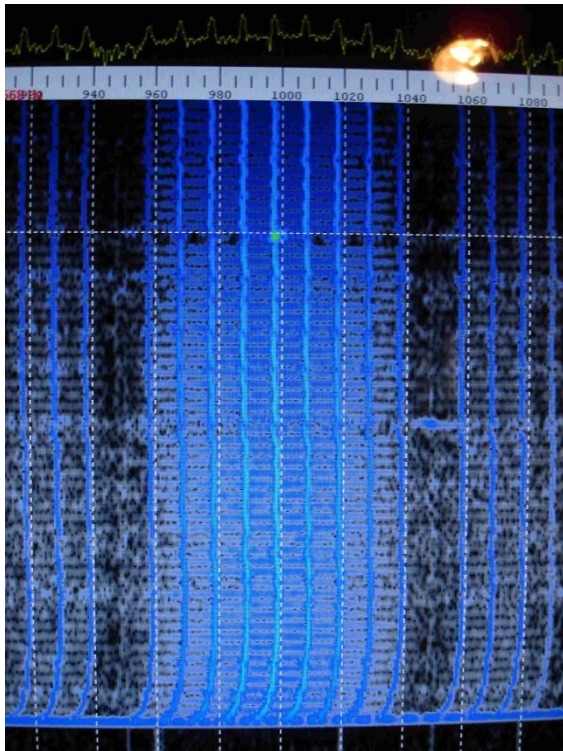

The initial drift during turn-on of the transceiver (just a few seconds) is visible at the bottom.

VFO Stabilizer for the Yaesu FT-707

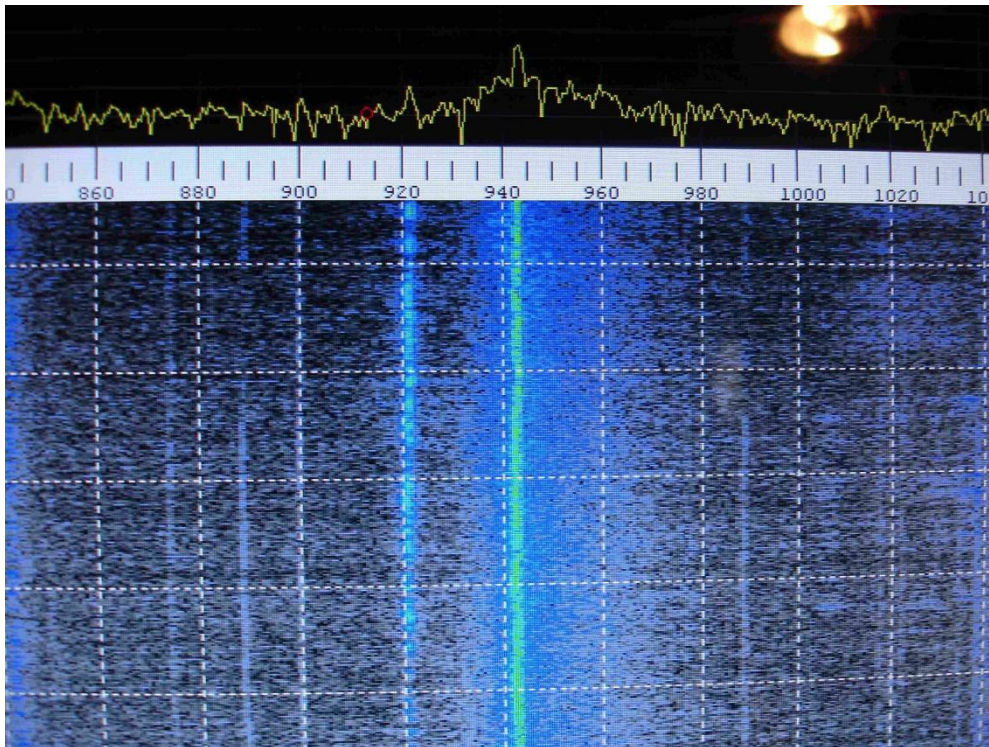Frequency stays put for hours and hours on end:



End of file